

# Logic Design ( Part 4)

## Sequential Logic - Latches


### (Chapter 3)

Based on slides © McGraw-Hill  
Additional material © 2013 Farmer  
Additional material © 2019 Narahari

1
 
### So Far: Combinational Logic

**MR. FORGETFUL**  
*By Roger Hargreaves*



#### Combinational Logic:

- Always gives the same output for a given set of inputs
- Aka “state-less” (i.e., no “state” or “memory”)

#### Sequential Logic:

- Its output depends on its inputs & its last output!
- Forms the basis for “state” or “memory” for a computer


2

2
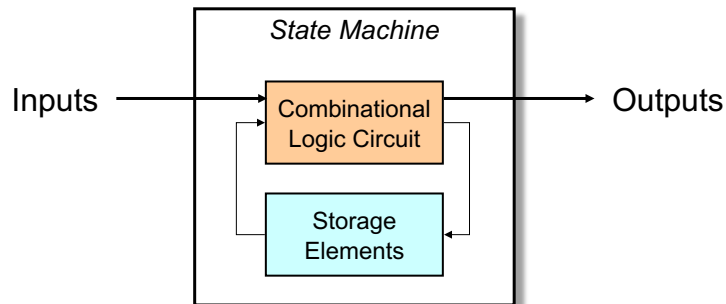
## (Finite) State Machine

type of sequential circuit

- Combines combinational logic with **storage**
- “Remembers” state, and changes output (and state) based on **inputs** and **current state**



3

3

## Sequential Logic: Starting point

- Where do we start: Build a device, using combinational logic devices, to **store** a value
  - RS Latch
    - Use this to build a more useful/easier to use latch – the D Latch
  - concept of memory
- Build it using the devices we have thus far
  - How ? Use “feedback” circuit
- What is the methodology behind design of sequential logic circuits
  - Finite State Machines
  - Example of Vending machine
- Combine sequential and combinational logic devices to “assemble” a simple processor!

4

4

## Feedback Circuits


- What happens if we feed the output of a combinational logic circuit to an input in the circuit?
  - This is the key to circuits that can store values!
- Stable circuit
  - Output point of circuit retains value indefinitely
- Unstable circuit
  - State that remains constant only for a duration of a few gate delays
- key takeaway: build stable circuits that can “hold” their value

5

5
 
## Feedback Circuits

- To retain their state values, sequential circuits rely on *feedback*.
- Feedback in digital circuits occurs when an output is looped back to the input.
- A simple example of this concept is shown below.
  - If Q is 0 it will always be 0, if it is 1, it will always be 1.



6

6

## Latches and Flip-Flops

- Latch: basic circuit for storage
  - Operate on changes in Level (i.e., 1 or 0)
- Flip-flop:
  - Sequential circuits take input from output of storage
  - Latches that work on change of level can lead to unstable sequential circuits
    - As level changes the outputs change --- inputs change!
  - Flip-Flop circuits designed to operate properly when they are part of a sequential circuit
  - Designed to work in a synchronized circuit with a Clock

7

7



## Most Basic Sequential Logic Circuit: R-S Latch

Most fundamental unit for static memory

- Has the ability to “store” its last output

R-S Latch – Cross-Coupled NAND gates

  - Output of each NAND gate serves as input to the other
- Two inputs: **S** (SET) & **R** (RESET)
- Two outputs: **Q** and **NOT(Q)** Recall:  $\text{NOT}(Q) = \sim Q = Q' = Q^{-}$
- Called a “Latch” because it can “Latch” onto data coming in



Another common way  
of drawing the same circuit

8

8

## R-S Latch

- The R-S latch is a bi-stable circuit which means that it can happily exist in either of two stable states. Just like a see-saw.
- You can push the latch from one state to another by setting or resetting it with the S-R signals
- The logic levels are maintained because of the feedback paths from outputs to inputs.



9

9



## Most Basic Sequential Logic Circuit: R-S Latch

Most fundamental unit for static memory

- Has the ability to “store” its last output

R-S Latch – Cross-Coupled NAND gates

  - Output of each NAND gate serves as input to the other
- Two inputs: **S** (SET) & **R** (RESET)
- Two outputs: **Q** and **NOT(Q)** Recall:  $\text{NOT}(Q) = \sim Q = Q' = Q^{-}$
- Called a “Latch” because it can “Latch” onto data coming in



Another common way  
of drawing the same circuit

10

10


## R-S Latch – Behavior/Truth Table

First, recall truth table for a NAND gate:

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

R-S Latch Operation:

- Best place to start is S=1, R=0

 

Next, look at top NAND gate

→ Its inputs are: 1 and 1

Blue 1, comes from lower NAND

→ Produces a 0 at its output

Therefore, when S=1, R=0

The output of latch is: Q=0, ~Q=1


11

## Most Basic Sequential Logic Circuit: R-S Latch

First, recall truth table for a NAND gate:

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

R-S Latch Operation:

 

Truth Table for R-S Latch:

ACTION	S	R	Q	~Q
	0	0		
	0	1		
RESET	1	0	0	1
	1	1		

Called the "RESET" action, as Q is set to 0

Also, notice: Q and ~Q opposite

12


## Most Basic Sequential Logic Circuit: R-S Latch

Truth table for a NAND gate:

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

Next, set S=1 R=1  
Check value of Q

R-S Latch Operation:

 

Truth Table for R-S Latch:

ACTION	S	R	Q	~Q
	0	0		
SET	0	1	?	?
RESET	1	0	0	1
HOLD	1	1	-	-
HOLD	1	1	0	1

HOLD's last value on its outputs!

OUTPUT depends on input and last output

13

## Most Basic Sequential Logic Circuit: R-S Latch


Truth table for a NAND gate:

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

Next, set S=0 R=1  
Check value of Q

R-S Latch Operation:

 - Next input case is called the "SET", when inputs are: S=0, R=1



1<sup>st</sup> look at upper NAND gate

→Its inputs are: 0 and X (anything)

→Produces a 1 at its output

Lower NAND gate

→Inputs are: 1 and 1

→Produces a 0 at its output

14


14

## Most Basic Sequential Logic Circuit: R-S Latch

Truth table for a NAND gate:

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

R-S Latch Operation:

 

Truth Table for R-S Latch:

ACTION	S	R	Q	~Q
	0	0		
SET	0	1	1	0
RESET	1	0	0	1
	1	1		

SETs LATCH to have a "1" at the output

15

## Most Basic Sequential Logic Circuit: R-S Latch


Truth table for a NAND gate:

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

R-S Latch Operation:

- Last valid input case is the "HOLD" S=1, R=1

 ➤ If we have just "SET" Latch, we will have Q=1, ~Q=0, already on outputs



Upper NAND gate

→ Has S=1 & former value of ~Q=0

→ Produces a 1 at its output

(same ~Q as when it started)

Lower NAND gate

→ Inputs are: 1 and 1

→ Produces a 0 at its output (same Q)

16




## Most Basic Sequential Logic Circuit: R-S Latch

Truth table for a NAND gate:

A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

Next, set S=1 R=1  
Check value of Q

R-S Latch Operation:

 


Truth Table for R-S Latch:

ACTION	S	R	Q	~Q
	0	0		
SET	0	1	1	0
RESET	1	0	0	1
HOLD	1	1	1	0

HOLD's value we "SET" last

17
 
## Storage - Cross-Coupled NANDs (R-S Latch)



Set value of Q by R=0 or S=0

Store value of Q with R=1, S=1

What happens with S=0 and R=0?

- Short answer: confusion
- Real circuits depend on both Q and ~Q
- Strange things may happen if both are 1

ACTION	S	R	Q	~Q
ILLEGAL	0	0	1	1
SET	0	1	1	0
RESET	1	0	0	1
HOLD	1	1	1	0
HOLD	1	1	0	1

D-Latches shows a way to prevent  
the RS Latch from ever getting S=R=0 as its input

18

18


## Gated D-Latch: Preventing “Illegal State” of RS Latch

### Add logic to an R-S latch

- Create a more convenient interface, prevent  $S=0$  &&  $R=0$
 
### Two inputs: D (data) and WE (write enable)

- When **WE = 1**, latch is set to **value of D**
  - $S = \text{NOT}(D)$ ,  $R = D$



19

## Circuits with Memory

- We now have a device (RS Latch) that is capable of storing a bit
  - It hold the previous value of Q
- but need to make sure the inputs are never  $R=S=0$
- Modify the circuit to get a D latch

20

20


## Gated D-Latch: Preventing "Illegal State" of RS Latch

### Add logic to an R-S latch

- Create a more convenient interface, prevent  $S=0$  &&  $R=0$
 
### Two inputs: D (data) and WE (write enable)

- When **WE = 1**, latch is set to **value of D**
  - $S = \text{NOT}(D)$ ,  $R = D$



21


## Gated D-Latch: Preventing "Illegal State" of RS Latch

### Add logic to an R-S latch

- Create a more convenient interface, prevent  $S=0$  &&  $R=0$
 
### Two inputs: D (data) and WE (write enable)


- When **WE = 1**, latch is set to value of D
  - $S = \text{NOT}(D)$ ,  $R = D$
- When **WE = 0**, latch continues to hold previous value
  - $S = R = 1$  (hold condition for SR latch)
- Extra logic does not allow  $S=0$ ,  $R=0$  case to occur



22
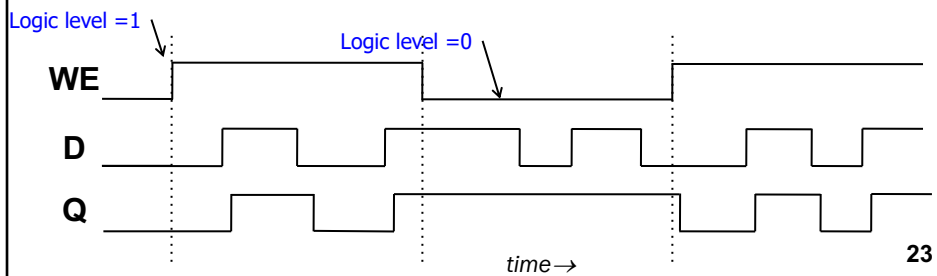
## D-Latch Timing Diagram

- The diagram below is called a “Timing” Diagram
  - Our D-Latch is previous-state dependent
    - We can think of this as a time dependency
    - Moving to the right on diagram, represents forward moving time
  - The inputs & outputs to our D-Latch are on left
    - Inputs/Outputs can be either “HIGH” (logic 1) or “LOW” (logic 0)
  - Think of this as a time-dependent truth table




23
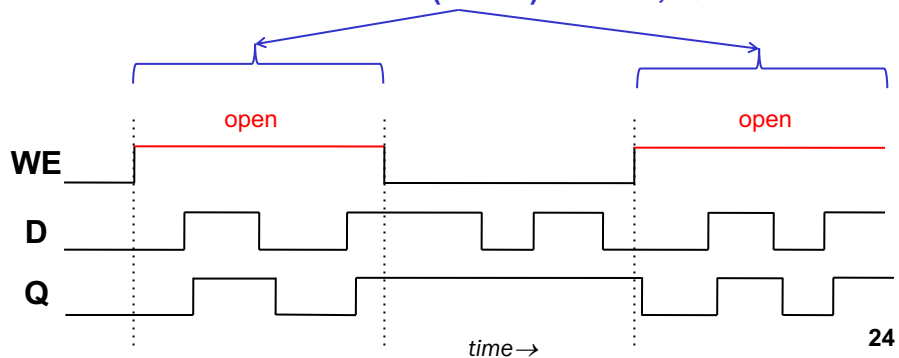
## D-Latch Timing Diagram

- When the WE signal is high the latch is said to be **open** and the output signal, Q, follows the input signal, D.
  - As in any combinational circuit there will be a small delay between the time that the input changes and the time that the output follows suit.

When latch is **OPEN** (WE=1): Notice, Q follows D




24
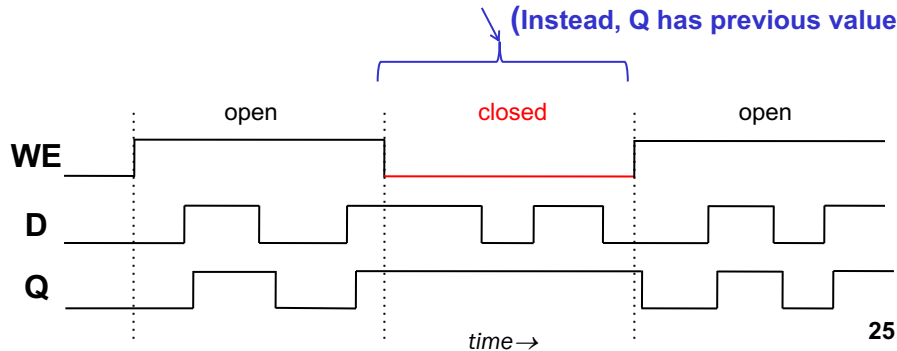
## D-Latch Timing Diagram

- When the WE signal is low the latch is **closed** and the output signal, Q retains its value.


When latch is **CLOSED (WE=0)**: Notice, Q doesn't follow D  
(Instead, Q has previous value)



25
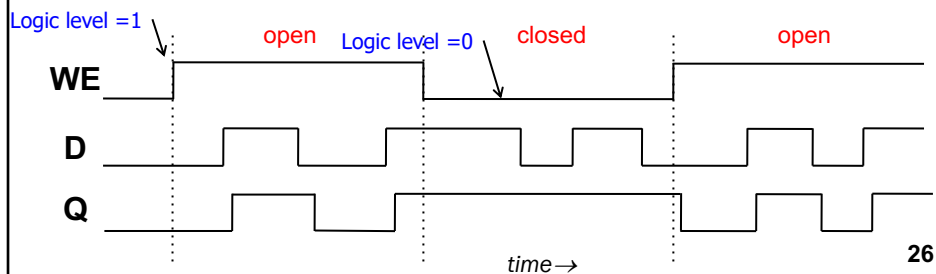
## D-Latch Timing Diagram

- Setup / Hold Times
  - The input signal should (D) be stable a certain amount of time before the WE signal is set to CLOSED (WE=0)
    - This is referred to as the **SETUP time**
  - In addition, the input signal (D) must be stable for a time after the WE is set to CLOSED (WE=0)
    - This is referred to as **HOLD time**
  - **Why?** Time must be given for inputs to propagate through NAND gates! Gates are not instantaneous!



26

## Next... Storage Devices

- Ok...we now have a device ( D-Latch) that can store a bit
- Use this to build 'real' storage devices....
- Temporary storage in a computer ?
  - Where are variables stored before being sent to the arithmetic unit for operations on them?
- Register
  - Can we build an n-bit register using latches?
- What about "main" memory
- Disk
  - Later...

27

27